

# Recent Development in High Power Capacitive Wireless Power Transfer



SAN DIEGO STATE  
UNIVERSITY

---

*Leadership Starts Here*

**Chris Mi, Ph.D, Fellow IEEE**

Professor and Chair, Dept. Electrical and Computer Engineering




Director, DOE GATE Center for Electric Drive Transportation

San Diego State University, (619)594-3741; mi@ieee.org

# Contents

- Introduction to SDSU
- Introduction of Wireless Power Transfer
- Double-sided LCLC Compensation Topology
- Capacitive Coupler Structure
- Prototypes and Experimental Results
- System Improvements
- Conclusion and Future Work

# San Diego State University

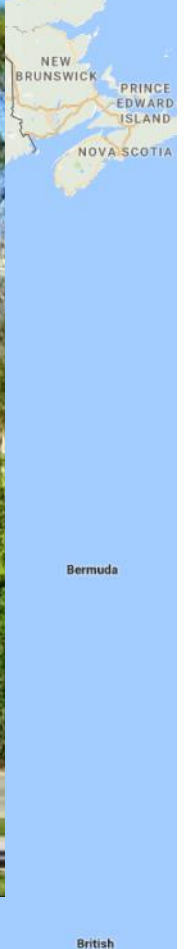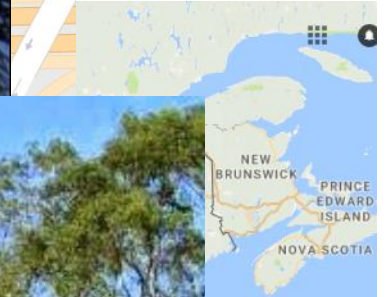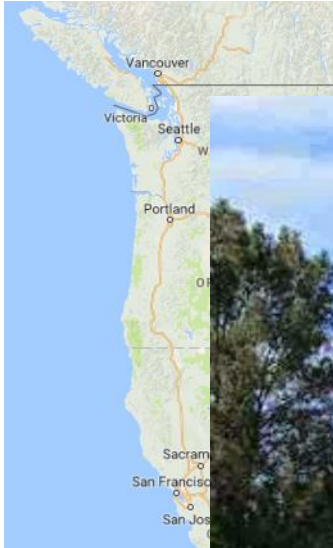


# Why WPT: Conductive Charging and Battery Swapping Have Some Issues

**Electric safety is of concern:  
electric shock due to rain, etc.**

**Charge station, plug and cable  
can be easily damaged, stolen**

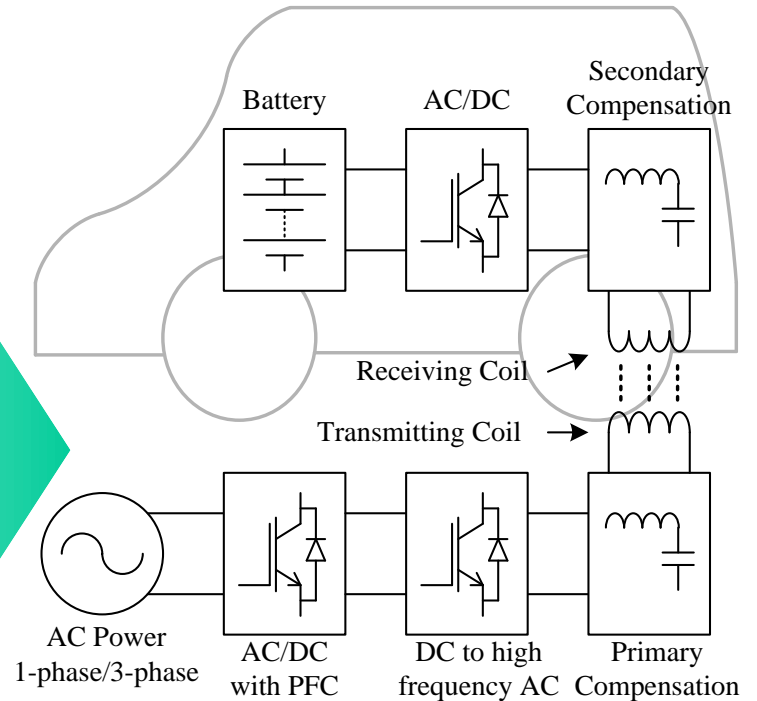**Charge/swap station takes a lot  
of space and affect the views**



**Possible Solution:  
Wireless Charging**

# History of Wireless Power Transfer

- 1830's: Faraday's law of induction
- 1890's: Tesla had a dream to send energy wirelessly
- 1990's: GM EV1 used an Inductive charger
- 2007: MIT demonstrated a system that can transfer 60W of power over 2 m distance at very low efficiency
- 2010: Wireless/inductive chargers are available: electronics, factories, medical
- 2012: Qualcomm, Delphi (Witricity), KAIST, etc. have developed EV wireless charger prototypes
- 2014: in-motion charging demonstration: Daejoen, Vienna, London



"Tesla Broadcast Tower 1904" by Unattributed(Life time: Unattributed) - Original publication: UnknownImmediate source: [http://www.sftesla.org/images/Tesla\\_Broadcast\\_Tower.JPG](http://www.sftesla.org/images/Tesla_Broadcast_Tower.JPG). Licensed under Public domain via Wikimedia Commons - [http://commons.wikimedia.org/wiki/File:Tesla\\_Broadcast\\_Tower\\_1904.jpeg#mediaviewer/File:Tesla\\_Broadcast\\_Tower\\_1904.jpeg](http://commons.wikimedia.org/wiki/File:Tesla_Broadcast_Tower_1904.jpeg#mediaviewer/File:Tesla_Broadcast_Tower_1904.jpeg)

The Predicted Wireless Charging Market: \$17 Billion by 2019, including applications in consumer electronics, home appliance, industrial robots, and EV charging



# Limitations of Current WPT

Safety of magnetic field




Low efficiency

Sensitive to vehicle alignment

High cost due to litz wire and ferrite

Large size


Limited distance

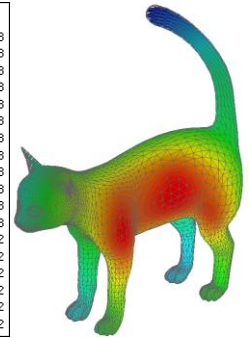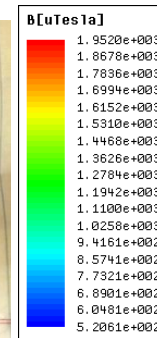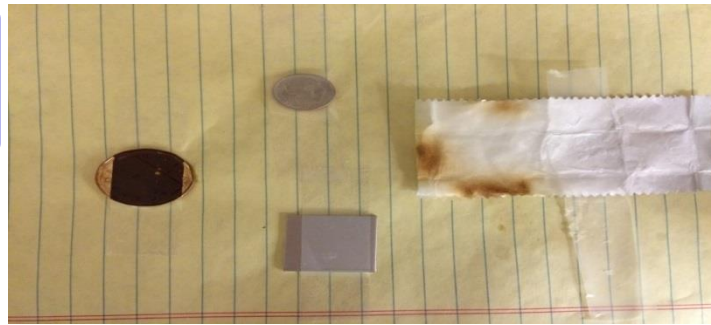

Need of:

- Novel designs
- Novel topologies
- Novel methods
- New materials
- New control methods


# Motivation: Disadvantages of IPT

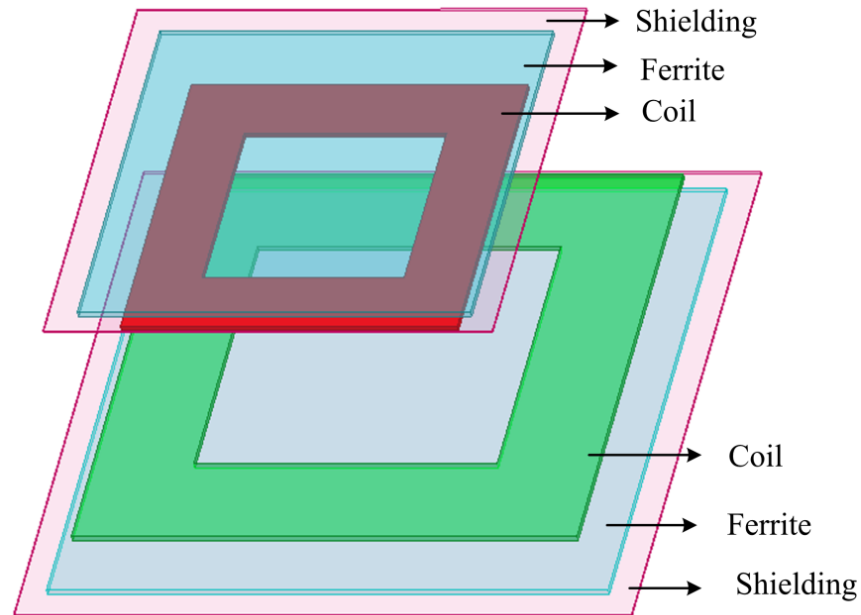


- Cost and Weight
  - Ferrite and Litz-wire are heavy and expensive
- Significant Eddy-Current Loss in Nearby Metals
  - Reduce system efficiency and cause temperature rise
- Misalignment Performance
  - System power drops rapidly with misalignment

# Analogy of CPT and IPT

- IPT System Structure

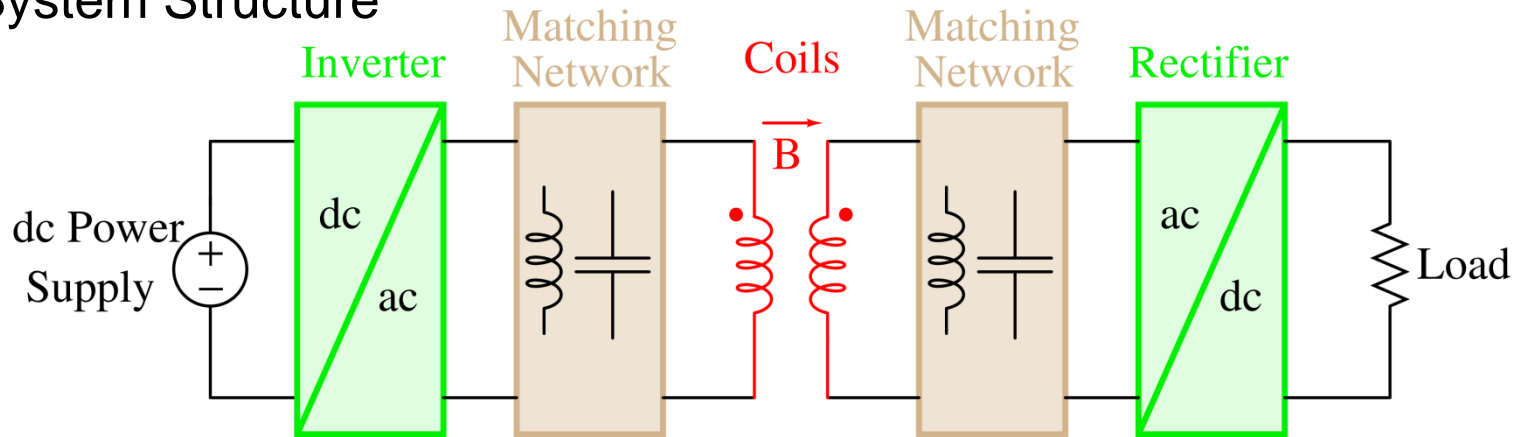

- CPT System Structure

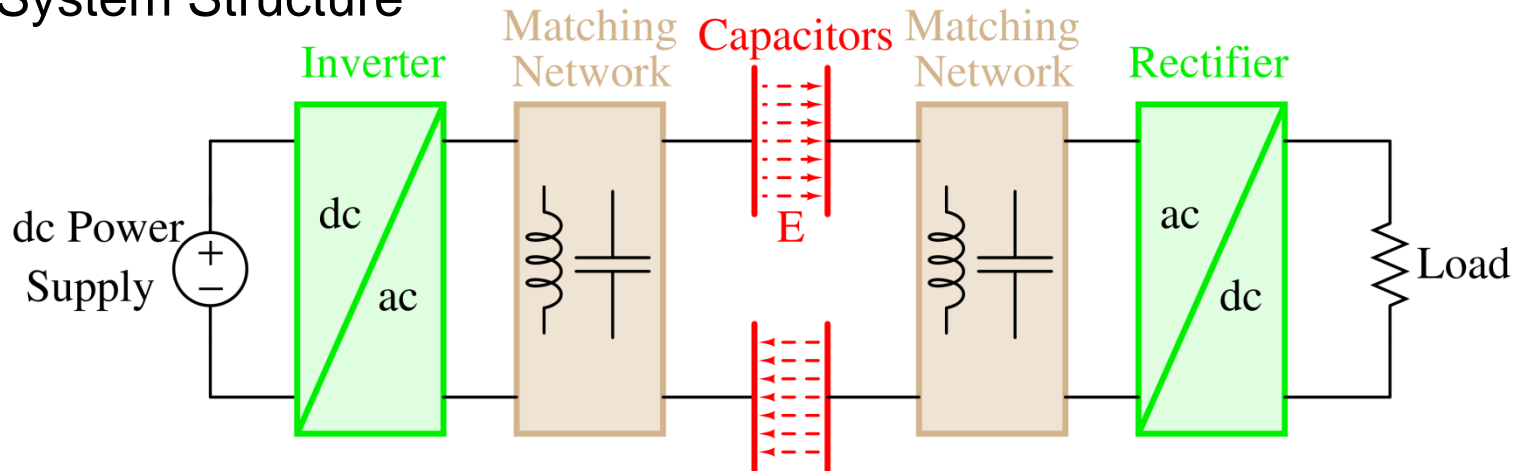

- Electric field is not sensitive to metal material nearby
- Electric field does not generate eddy-current loss in the metal
- CPT coupler uses metal plates, instead of Litz-wire, reduce system cost



# Challenges of CPT for EV Charging


- Small Coupling Capacitance

- An Example:
- Plates Size  $l_1=610\text{mm}$  (24in)
- Distance  $d=150\text{mm}$
- Coupling capacitance of parallel plates is<sup>[8]</sup>:

$$C_s = [1 + 2.343 \cdot (d / l_1)^{0.891}] \cdot \frac{\epsilon \cdot l_1^2}{d} = 36.7\text{pF}$$


- The former compensation topologies are not suitable to transfer **HIGH** power with so **SMALL** coupling capacitance

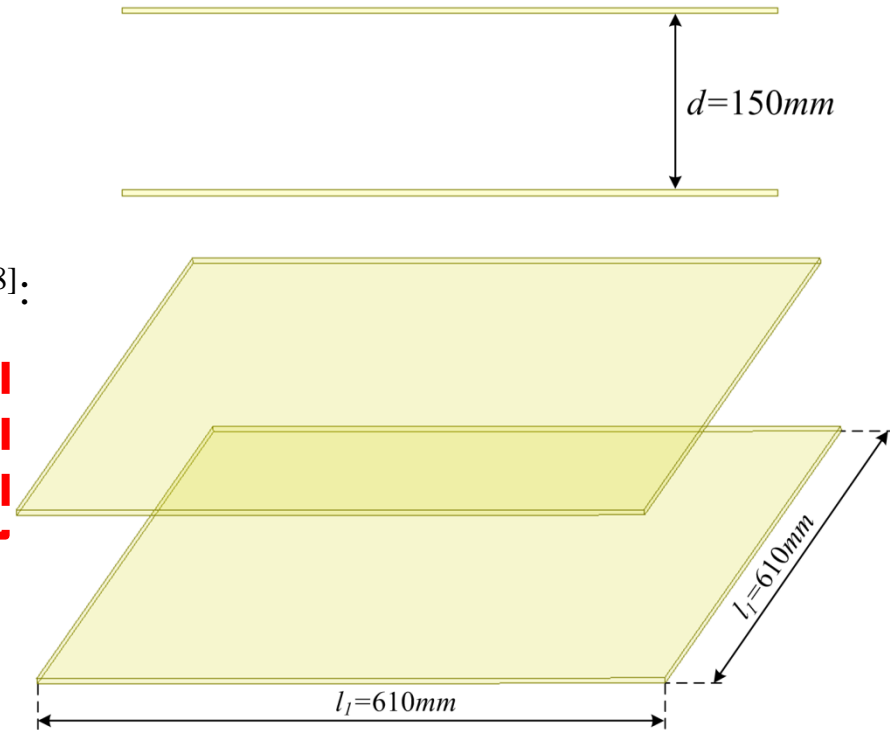- Series or parallel topology: requires too large inductance or too high switching frequency



**NEW Compensation Topology is Required!**


# Double-sided LCLC Circuit Topology

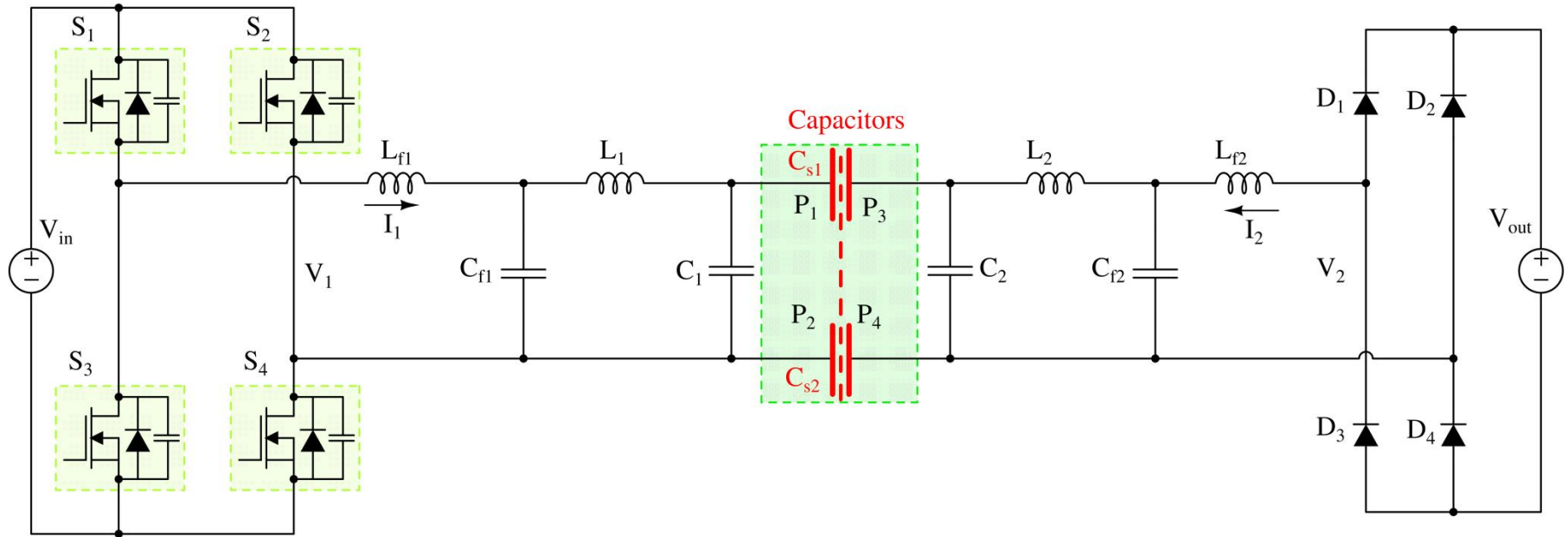

- Two inductors and two capacitors are used at each side
- $P_1$  and  $P_2$  are at the primary side,  $P_3$  and  $P_4$  are at the secondary side
- $P_1$  and  $P_3$  form a coupling capacitor,  $P_2$  and  $P_4$  form the other capacitor

F. Lu, H. Zhang, H. Hofmann and C. Mi, "A Double-Sided LCLC-Compensated Capacitive Power Transfer System for Electric Vehicle Charging," in *IEEE Transactions on Power Electronics*, vol. 30, no. 11, pp. 6011-6014, Nov. 2015.  
doi: 10.1109/TPEL.2015.2446891

# System Power of FHA Analysis

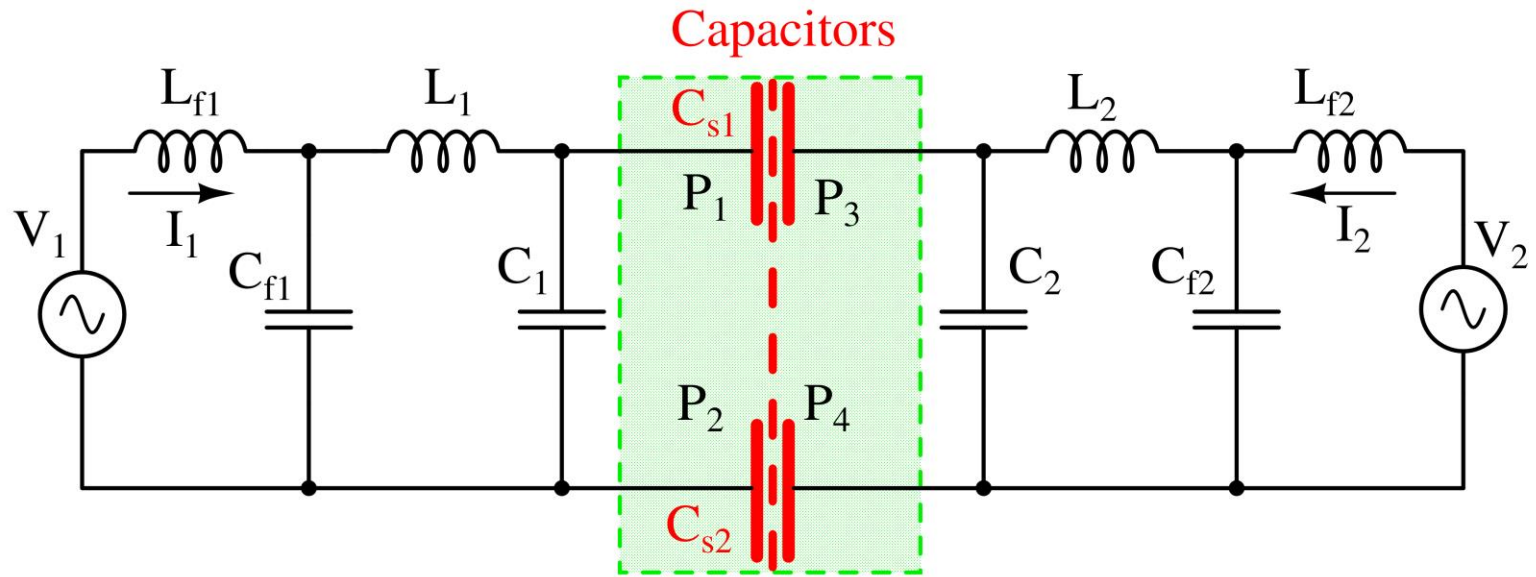

- At input inverter side,  $V_1$  and  $I_1$  are in phase
- At output rectifier side,  $V_2$  and  $(-I_2)$  are in phase
- Neglect passive components losses, the system power is expressed as:

$$P_{in} = P_{out} = \frac{\omega_0 C_s \cdot C_{f1} C_{f2}}{C_1 C_2 + C_1 C_s + C_2 C_s} \cdot V_1 \cdot V_2 = \frac{\omega_0 C_s \cdot C_{f1} C_{f2}}{C_1 C_2 + C_1 C_s + C_2 C_s} \cdot \frac{2\sqrt{2}}{\pi} \cdot V_{in} \cdot \frac{2\sqrt{2}}{\pi} \cdot V_{out}$$

- If there exists  $C_{1,2} \gg C_s$



$$P_{in} = P_{out} \approx \omega_0 C_s \cdot \frac{C_{f1} C_{f2}}{C_1 C_2} \cdot \frac{2\sqrt{2}}{\pi} \cdot V_{in} \cdot \frac{2\sqrt{2}}{\pi} \cdot V_{out}$$

# Parameter Design and Simulation

➤ A 2.4kW CPT system is designed with parameters in the following table.

$V_{in}$	$V_{out}$	$f_{sw}$	$L_{f1} (L_{f2})$	$C_{f1} (C_{f2})$	$C_1 (C_2)$	$C_{s1}(C_{s2})$	$L_1$	$L_2$
265V	280V	1MHz	11.6 $\mu$ H	2.18nF	100pF	36.7pF	231 $\mu$ H	242 $\mu$ H

➤ Circuit simulation is shown below

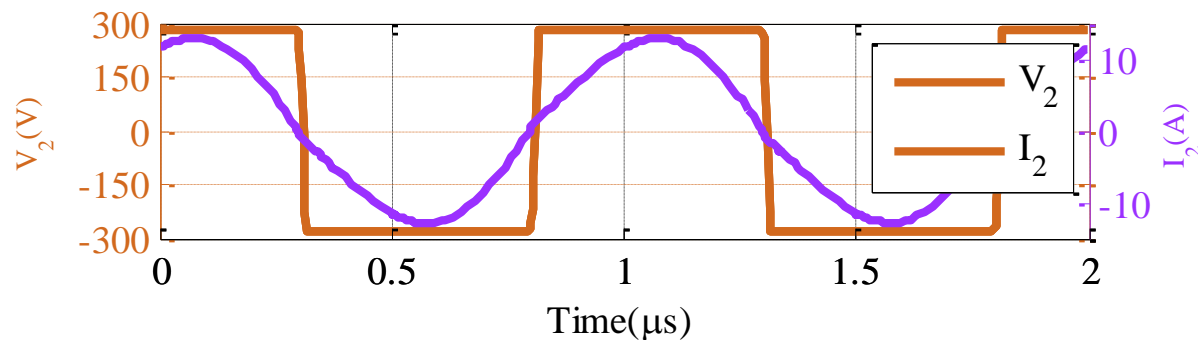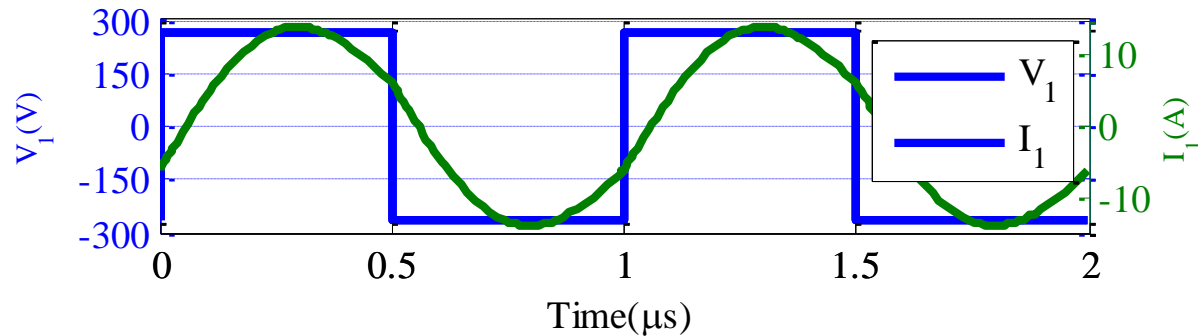


# Voltage and Current Stress

- Voltage and current stress are calculated by the previous FHA analysis

Components	$L_{f1} (L_{f2})$	$C_{f1} (C_{f2})$	$C_1 (C_2)$	$L_1(L_2)$	Plates
Voltage	1.0 kV	1.0 kV	7.2 kV	7.2 kV	3.2 kV
Current	15.5 A	15.0 A	4.8 A	5.2 A	0.7 A

- Inductors are wound with multiple turns to reduce voltage stress between turns
- Multiple capacitors are connected in series to form  $C_1$  and  $C_2$
- Multiple capacitors are connected in parallel to form  $C_{f1}$  and  $C_{f2}$
- The electric field in this system is 3.2kV/150mm, and the breakdown field of air is about 3.0kV/mm. Therefore, there is no concern of arcing

# Prototype Design


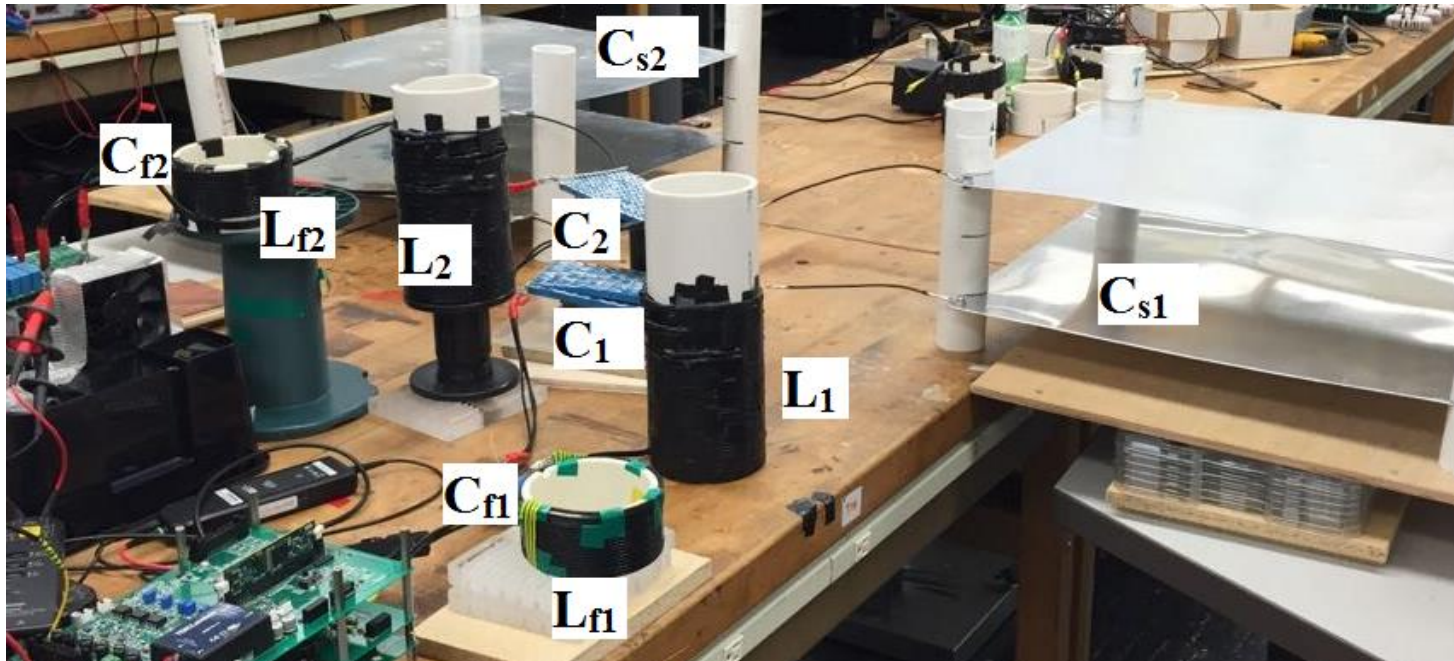


- Plates are made by aluminum sheets
- Inductors are wound by AWG46 Litz-wire without magnetic core
- High-power-frequency thin film capacitors resonate with the inductors
- Silicon Carbide (SiC) MOSFETs C2M0025120D are used in the inverter
- SiC diodes IDW30G65C5 are used in the rectifier



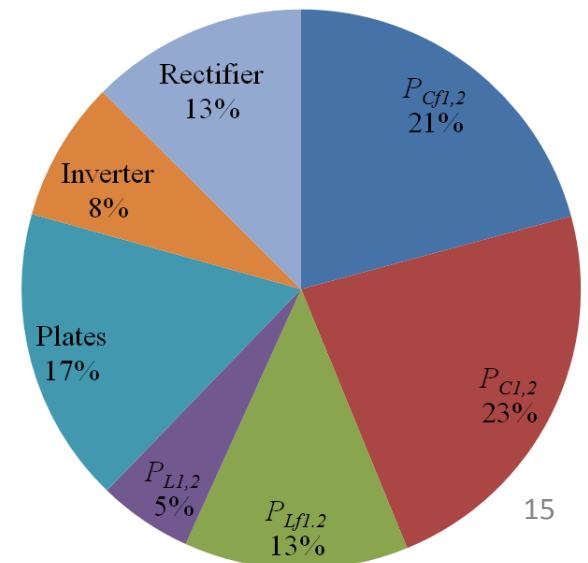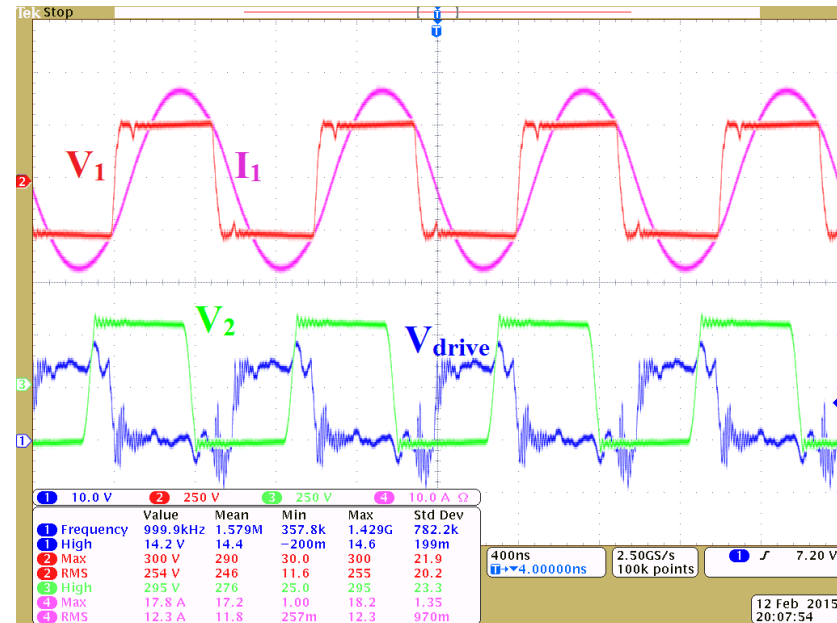
# Experimental Results

- $P_{out}=2.4\text{kW}$  at designed input/output
- The experimental waveform is the same with the simulations
- Soft-switching is achieved
- There is high frequency noise on the driver signal
- Most of the power losses distribute on the capacitors and plates
- If the inductors are wound on magnetic core, the system efficiency will drop 1%-3%.



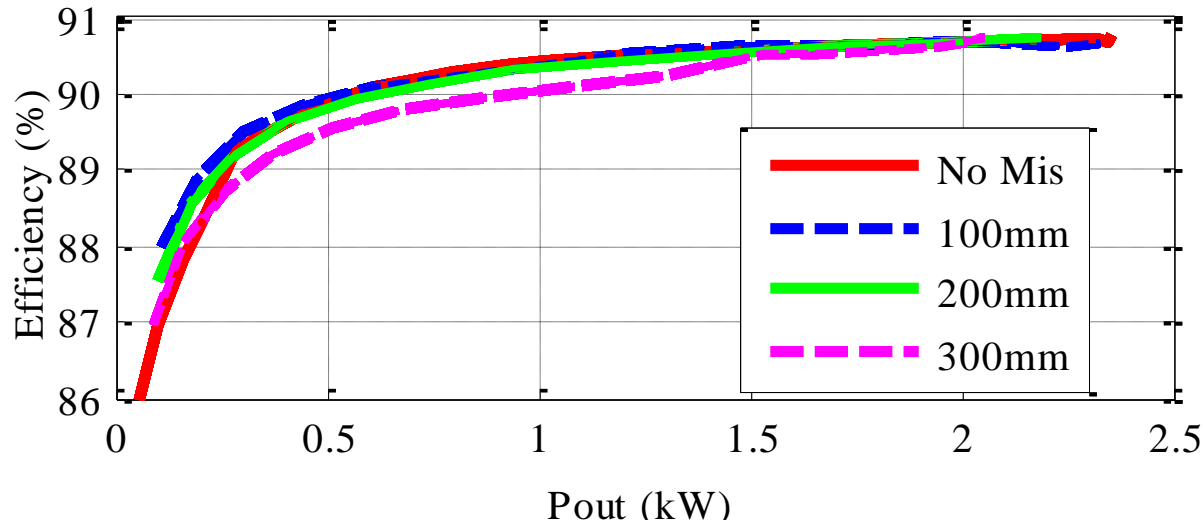
# Tolerance to Misalignment and Distance

- Output Power maintains 2.1 kW at 300 mm X axis misalignment




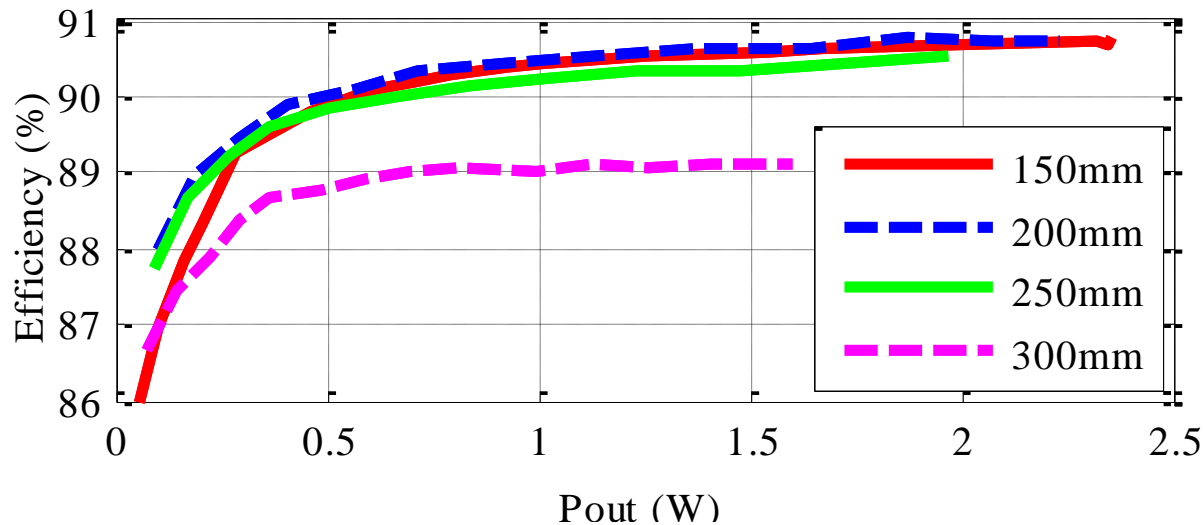- Output Power maintains 1.7 kW at 300 mm Z axis distance



# Potential Improvements


# LCL Compensation Topology

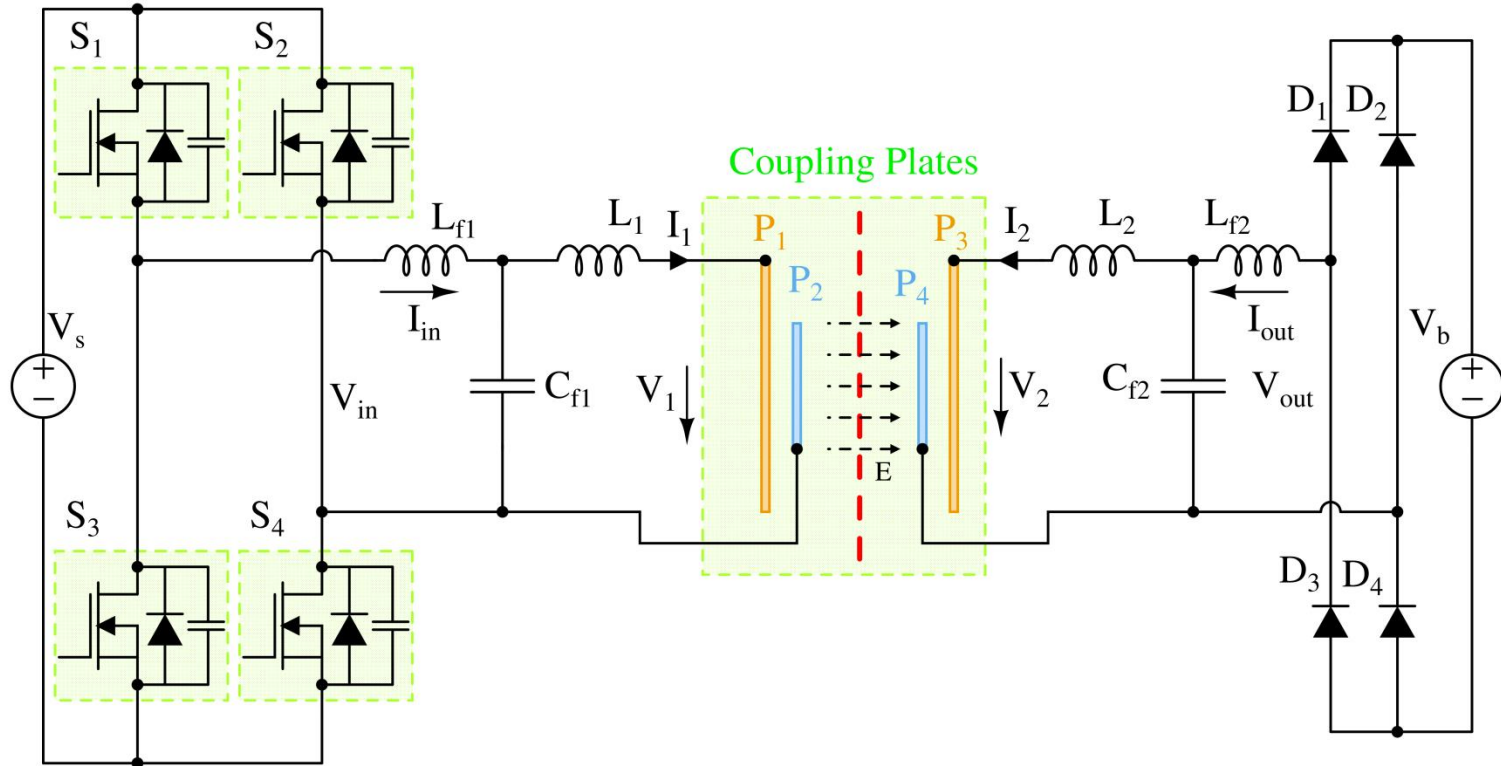

- Compensation topology is simplified and The LCL compensation circuit is used to resonate with the plates, instead of the LCLC topology

H. Zhang; F. Lu; H. Hofmann; W. Liu; C. Mi, "A 4-Plate Compact Capacitive Coupler Design and LCL-Compensated Topology for Capacitive Power Transfer in Electric Vehicle Charging Applications," in *IEEE Transactions on Power Electronics* , vol.PP, no.99, pp.1-1; doi: 10.1109/TPEL.2016.2520963

# IPT+CPT Combined System


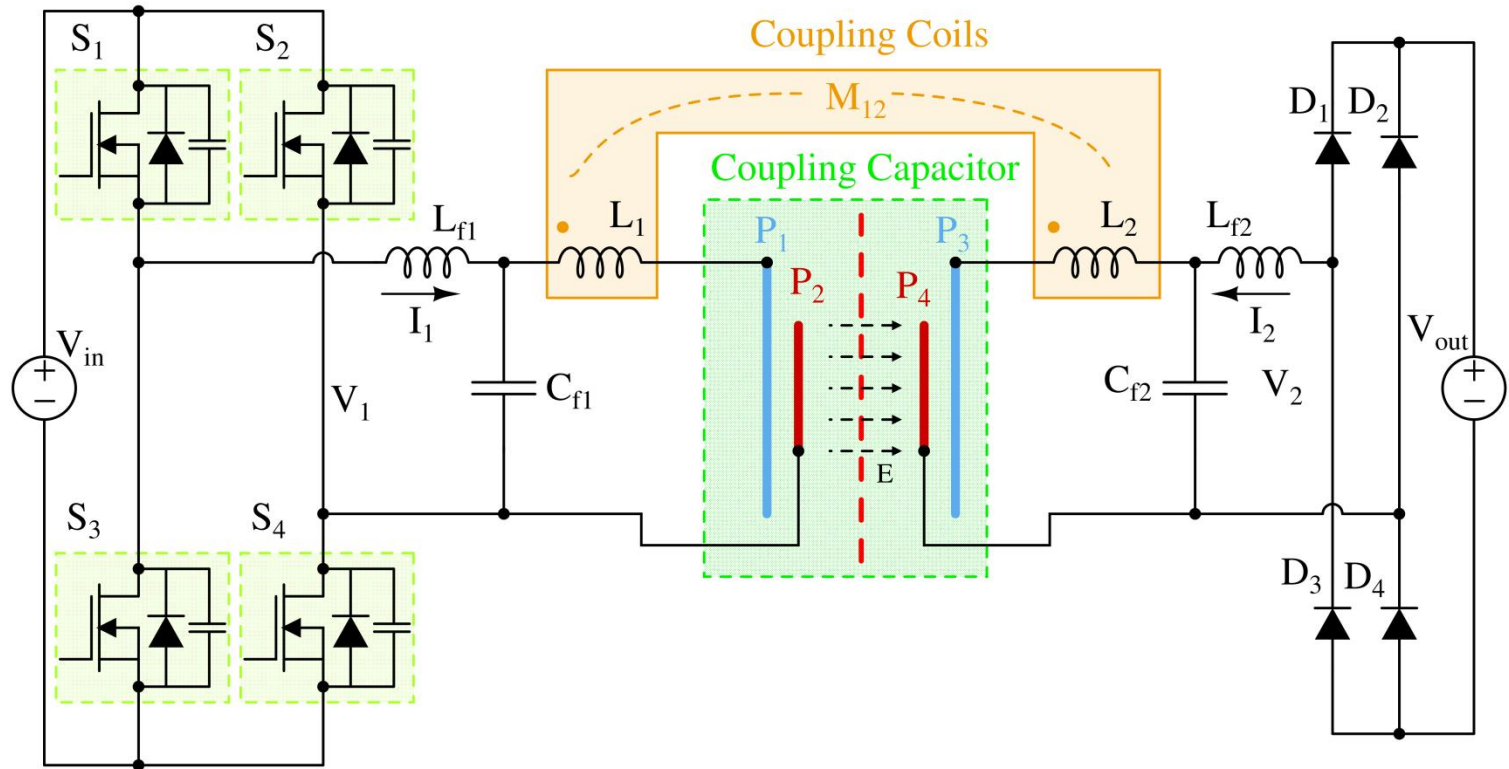


- The two inductors  $L_1$  and  $L_2$  are inductively coupled
- The system utilizes both electric and magnetic fields to transfer power

F. Lu; H. Zhang; H. Hofmann; C. Mi, "An Inductive and Capacitive Combined Wireless Power Transfer System with LC-Compensated Topology," in *IEEE Transactions on Power Electronics*, vol. PP, no. 99, pp. 1-1, doi: 10.1109/TPEL.2016.2519903
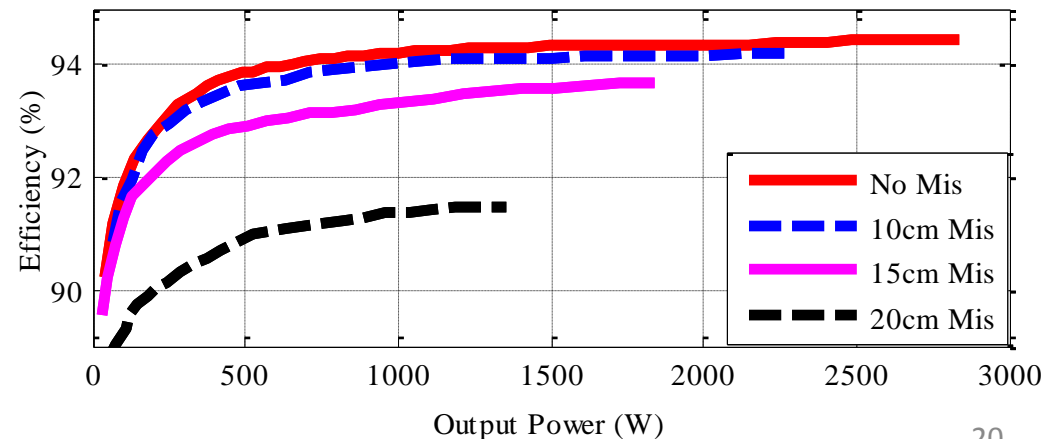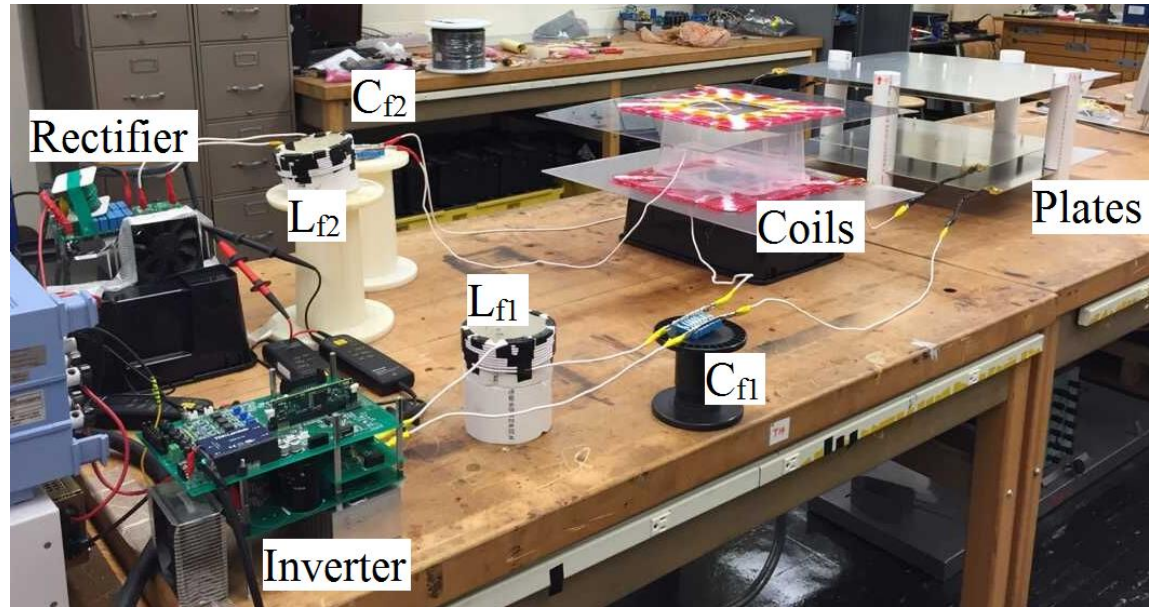
# Experiments of IPT+CPT Combined System

- Coil size:  $320 \times 320\text{mm}$
- Plate size:  $610 \times 610\text{mm}$
- Only LC compensation network is required at each side
- At nominal input and output condition,  
 $P_{IPT}=2000\text{W}$ , and  
 $P_{CPT}=800\text{W}$
- The system also has good misalignment ability





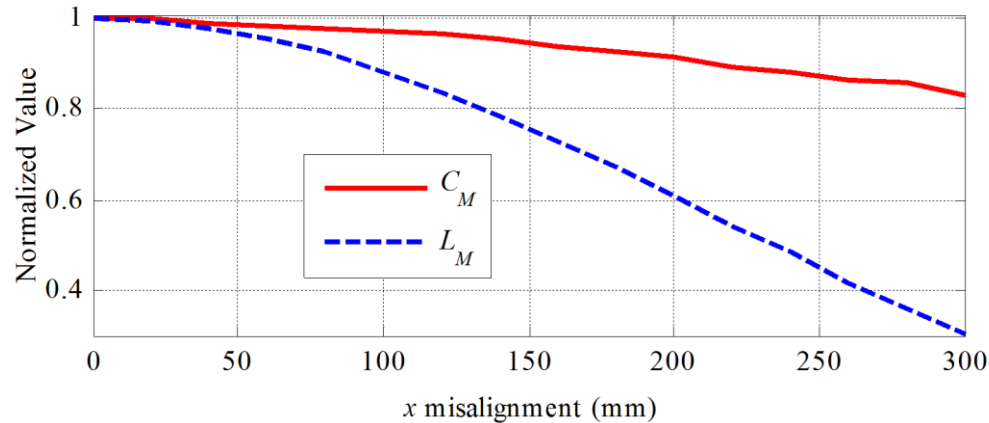
# Misalignment Performance


- x Direction Misalignment

Advantage: Better Misalignment Performance



- $C_M$  remains 84.2% of the well-aligned value,  $L_M$  remains 30% of the well-aligned value

- Air-gap Variation

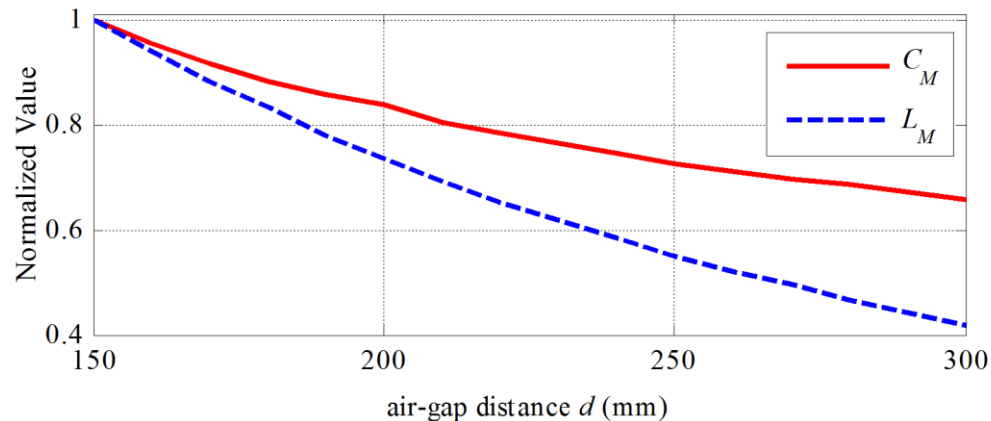


- $C_M$  remains 66.5% of the well-aligned value,  $L_M$  remains 41% of the well-aligned value

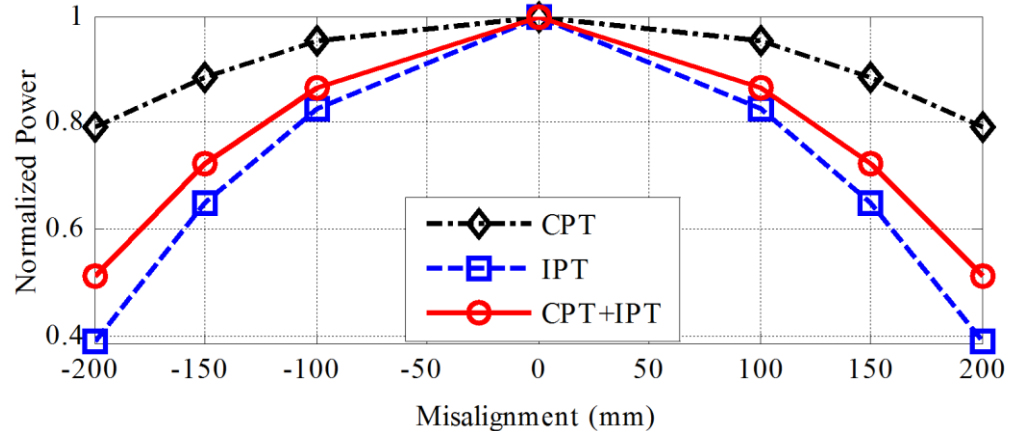
# Misalignment Performance

- Output Power

Advantage:  
Compared to an IPT  
system,  
misalignment  
performance is improved



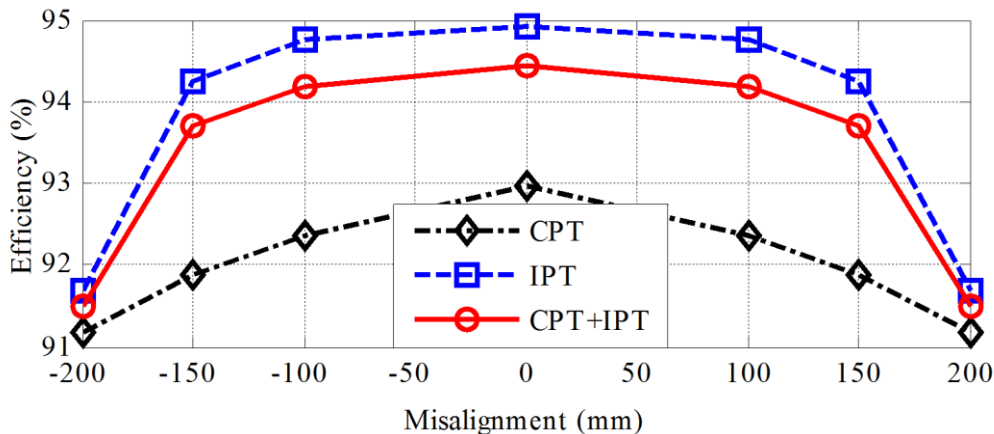- Output power drops to 1.35 kW at 200 mm misalignment (47.5% of well-aligned power)




- Efficiency

Advantage:  
Compared to a CPT  
system,  
efficiency is improved


- DC-DC efficiency remains higher than 91.5%

# Dynamic Capacitive Power Transfer [11]

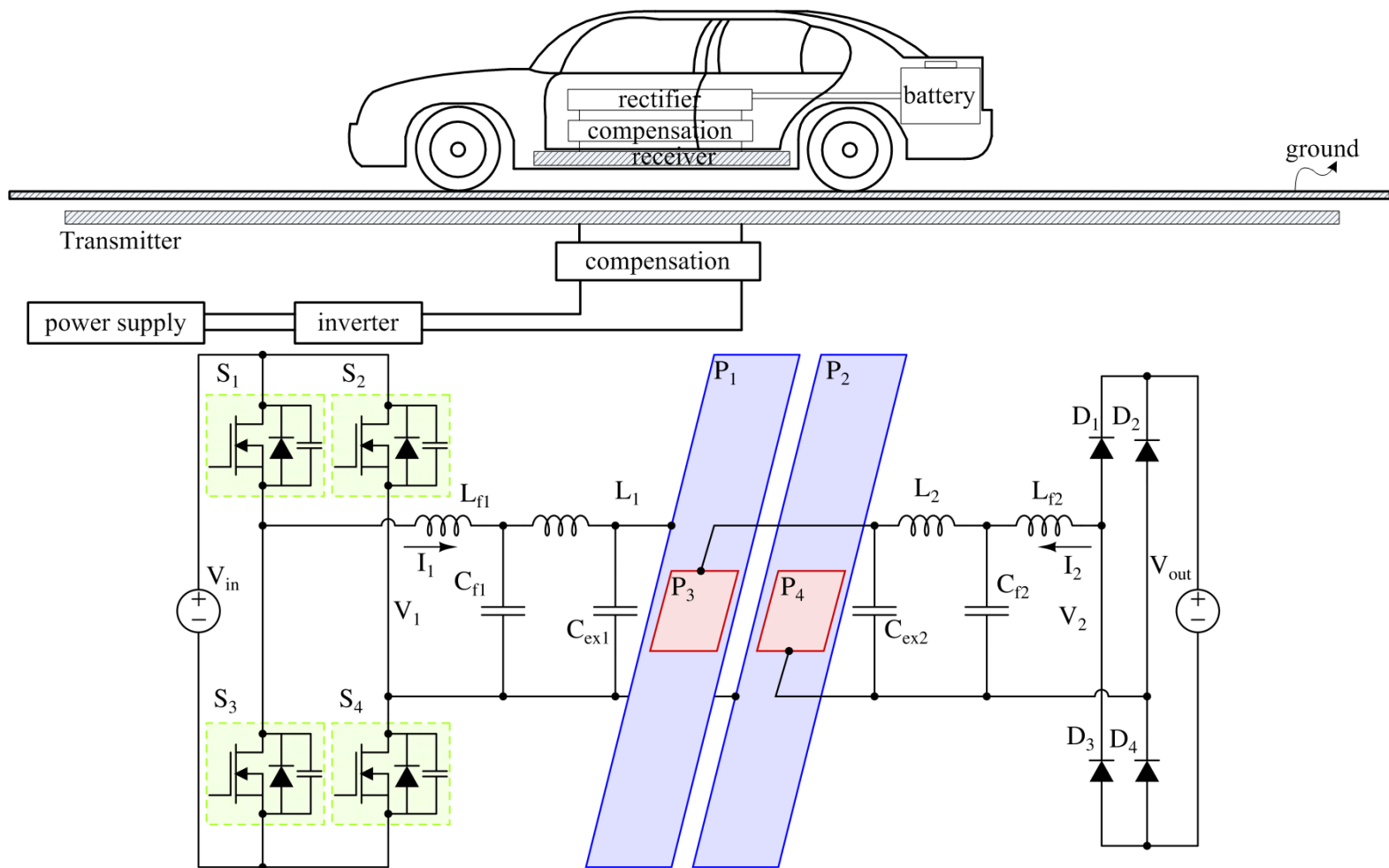


- Reduce system cost using metal plates as capacitive couplers
- Reduce stand-by power loss because of small circulating current in the coupler

# Experimental Prototype

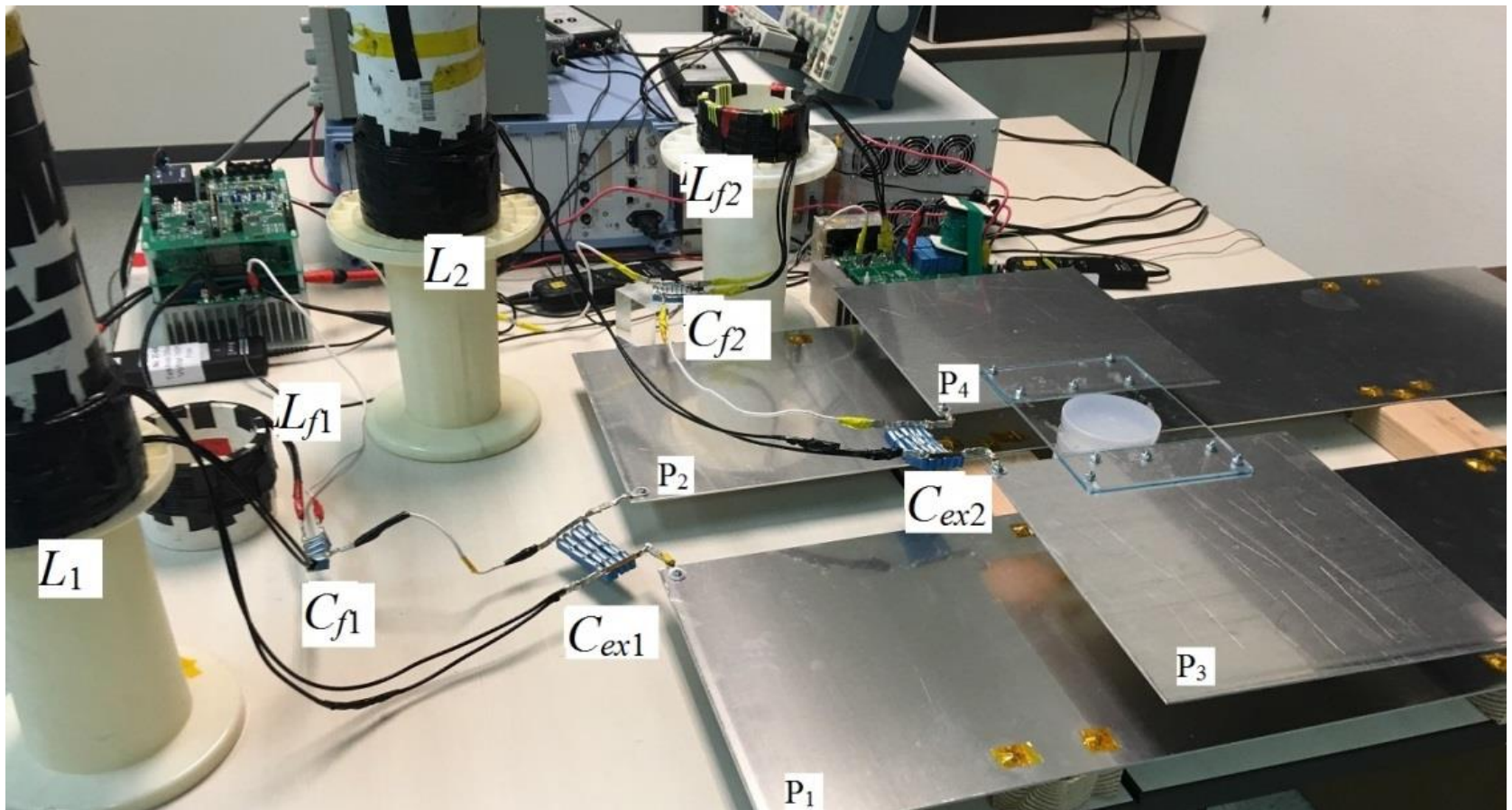

- Transmitter size: 1200mm×300mm
- Receiver size: 300mm×300mm
- Airgap distance: 50mm


# LC Compensated CPT Repeater System

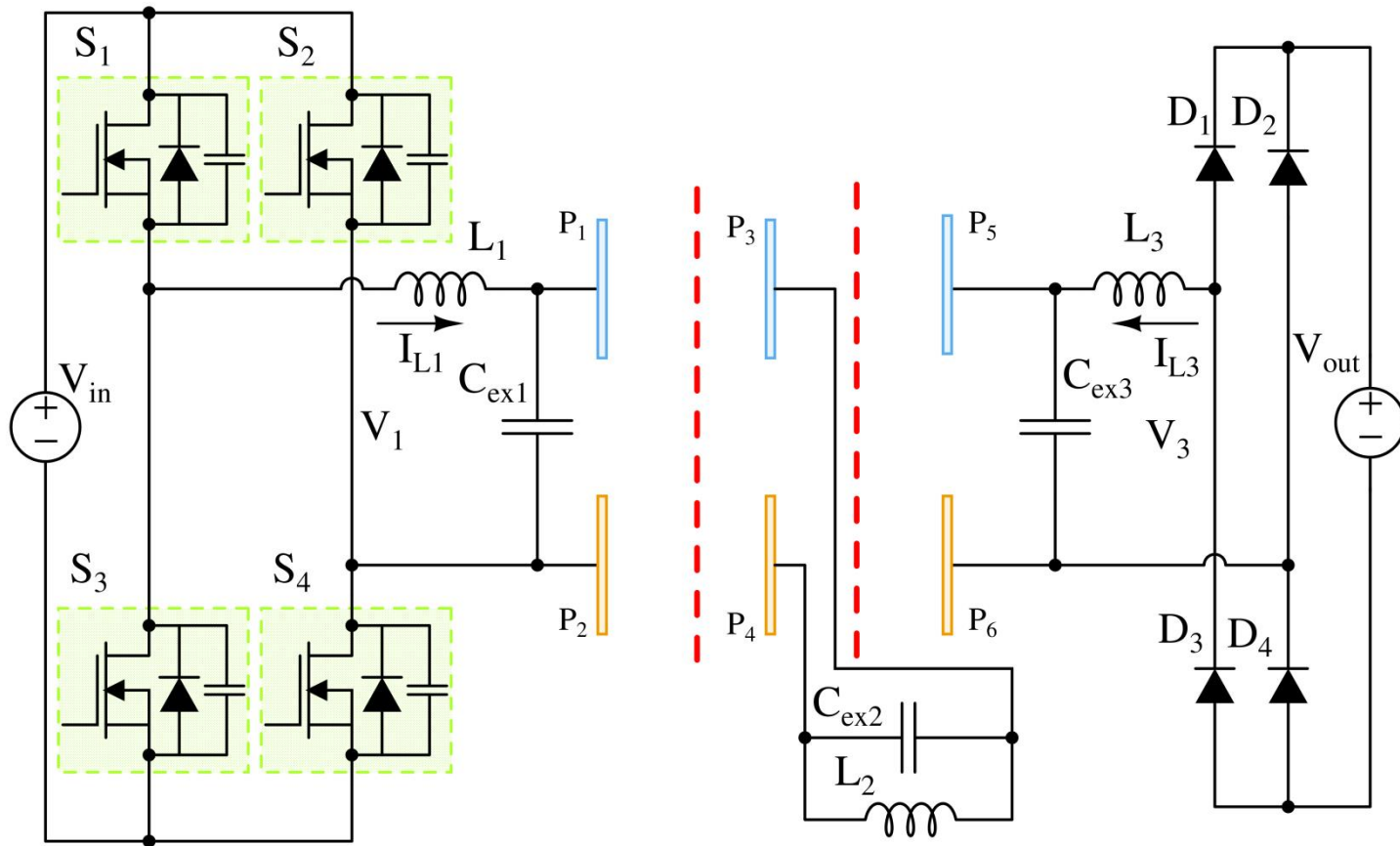

- LC compensation circuitry compensate the capacitive coupler
- Parameters are designed to achieve resonances




# 100W Prototype

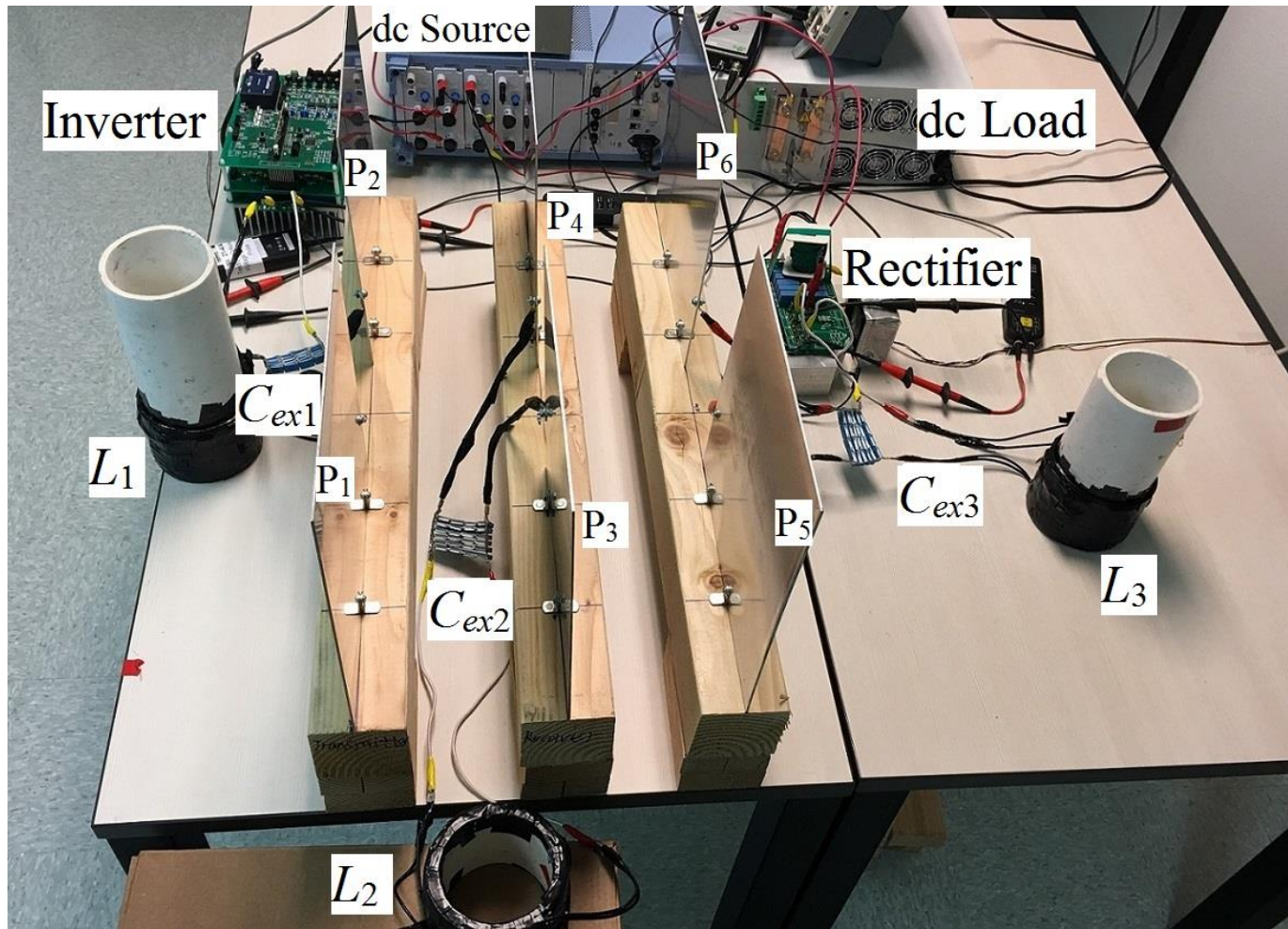


- Aluminum plates are used to make capacitive coupler
- Transfer distance is 180mm + 180mm



# Single Ended CPT System

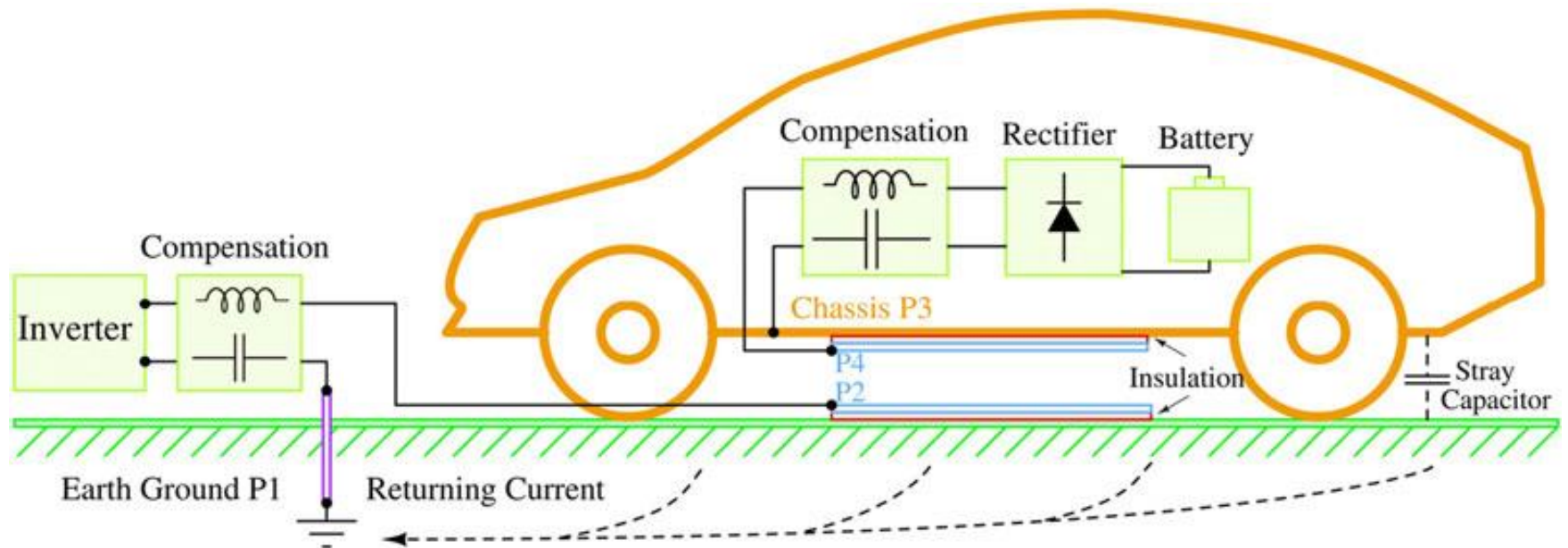


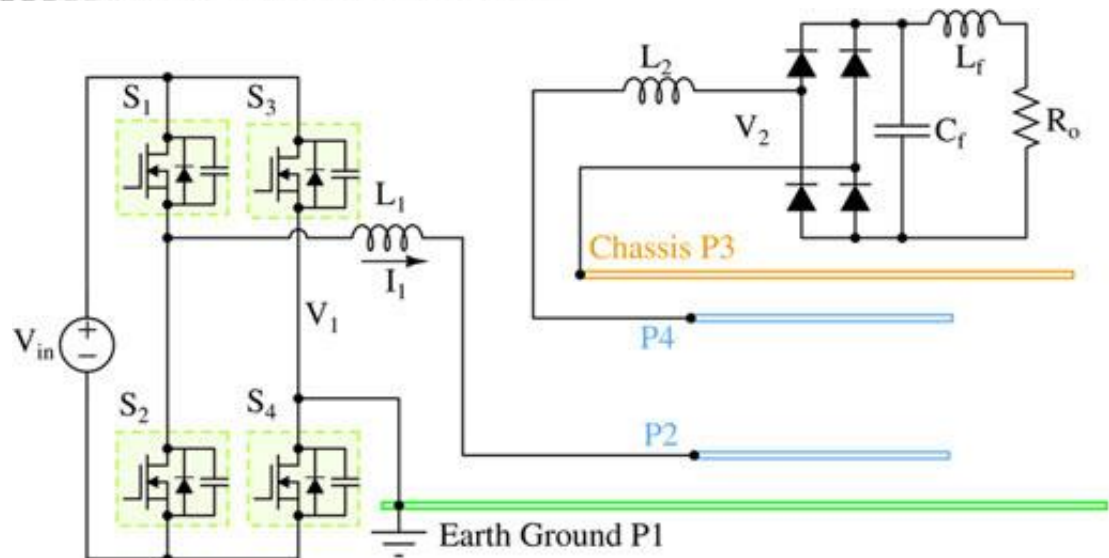- Two plates only
- Chassis and the earth are the third and fourth plates




# Safety Issue and Impact of Foreign Object

- High voltages on plates

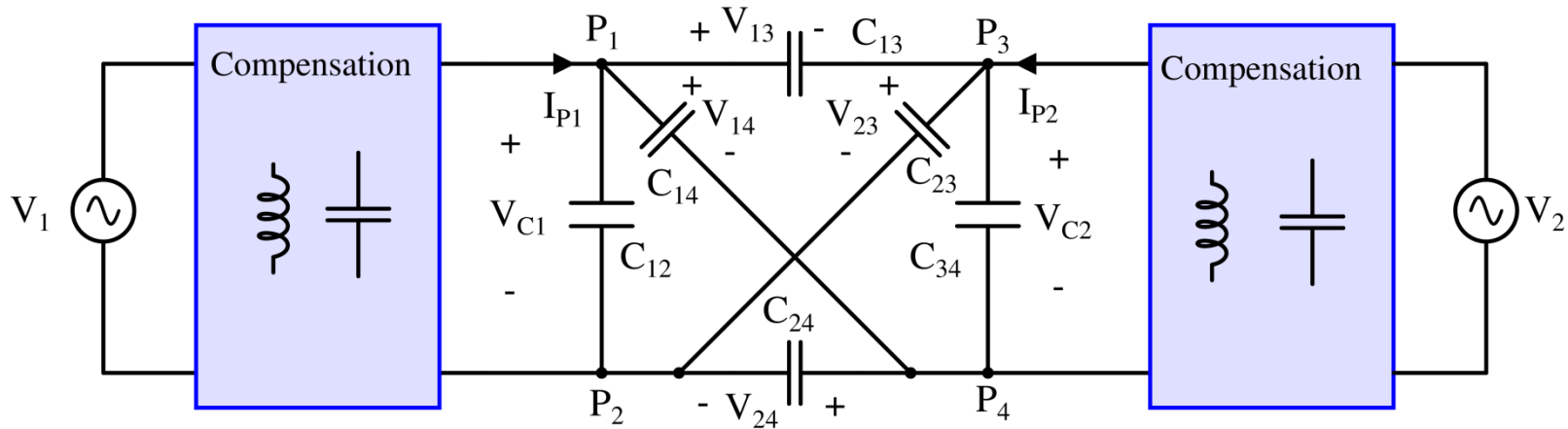

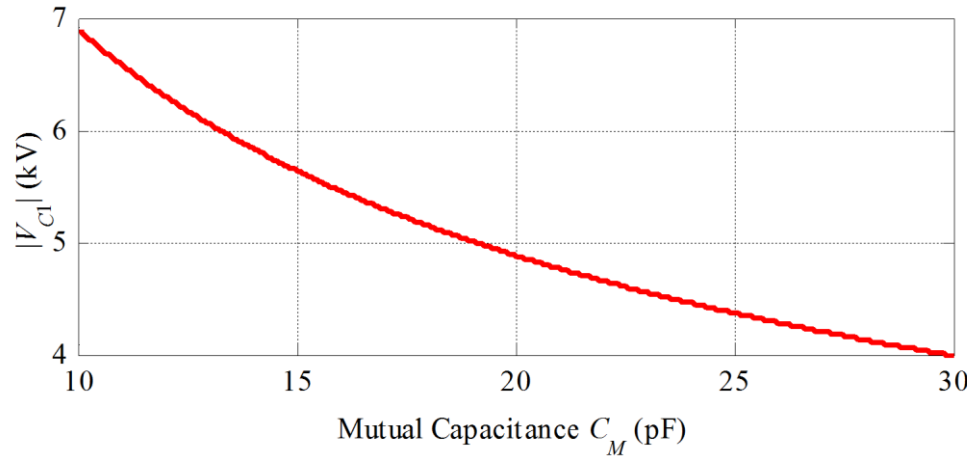- An example:  $P_M = 3.0\text{kW}$ ,  $f_{sw} = 1\text{MHz}$




$$P_M = \omega C_M \cdot |V_C|^2$$

$$|V_{C1}| = \sqrt{\frac{P_M}{\omega C_M}}$$

- Voltages are in kV level
- Solution: reliable insulation is required on plate surface


# Electric Field Emissions

- $|V_{C1}|=|V_{C2}|=5.2$  kV,  $|V_{14}|=|V_{23}|=4.2$  kV, and  $|V_{13}|=|V_{24}|=3.1$  kV

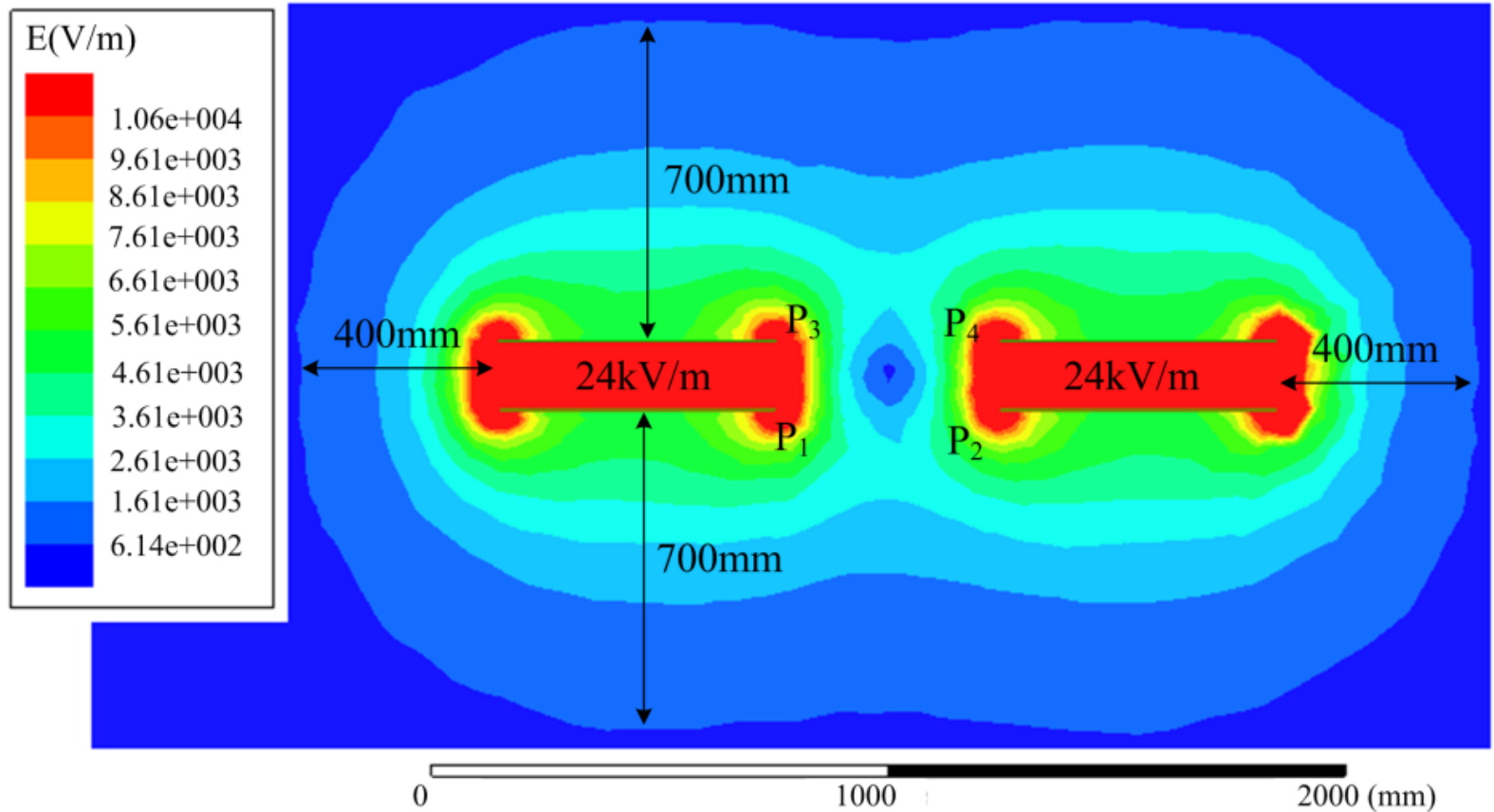



- Safe range is  $700 \text{ mm}$  from the edge of plates
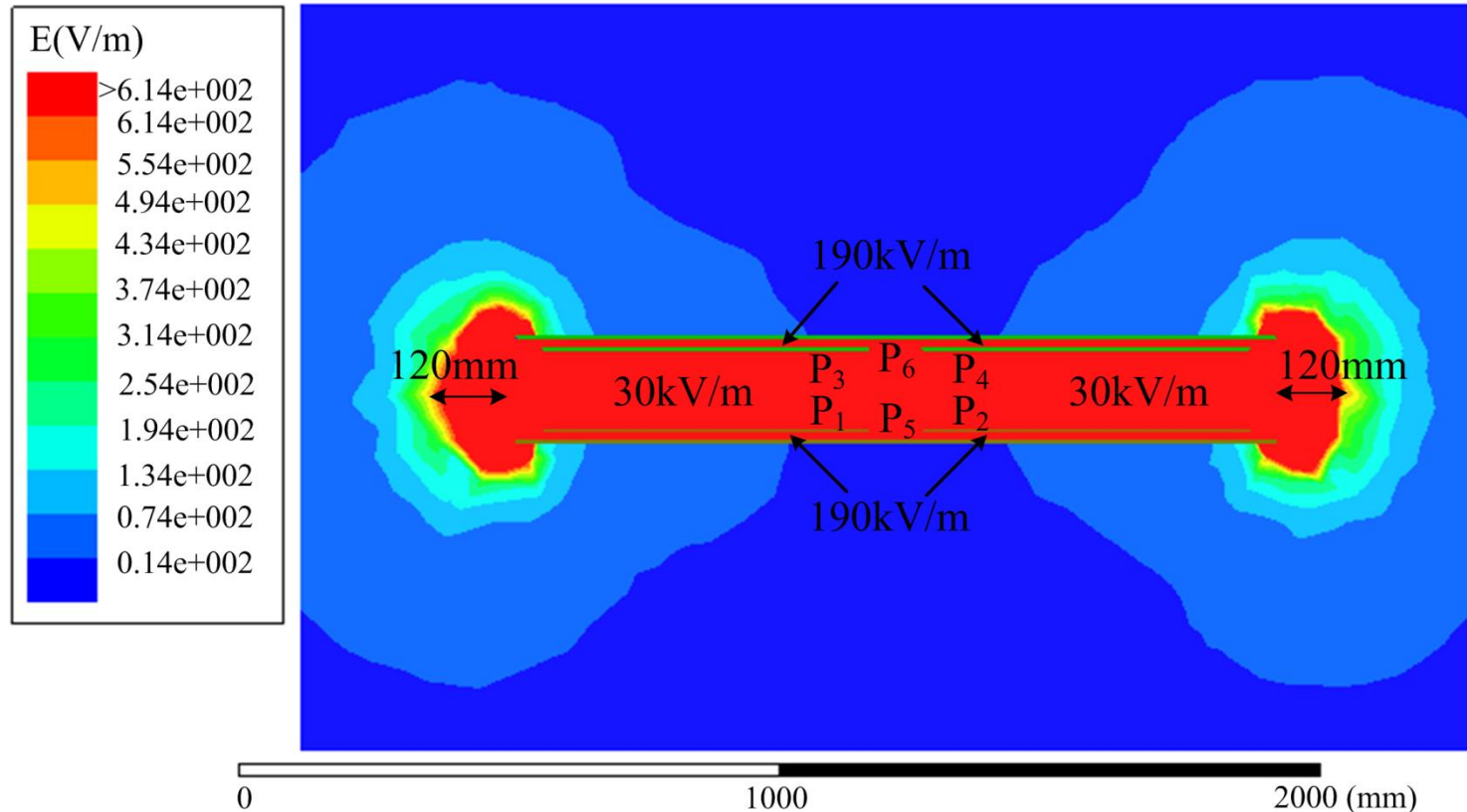
# Solution: Six-Plate Coupler<sup>[12]</sup>




- $P_5$  is grounded, and  $P_6$  is equivalently grounded
- Safe range is  $120 \text{ mm}$  from the edge
- Further research shows safe range is  $400 \text{ mm}$  from the edge with  $300 \text{ mm}$  misalignment

# Metallic Foreign Object Influence

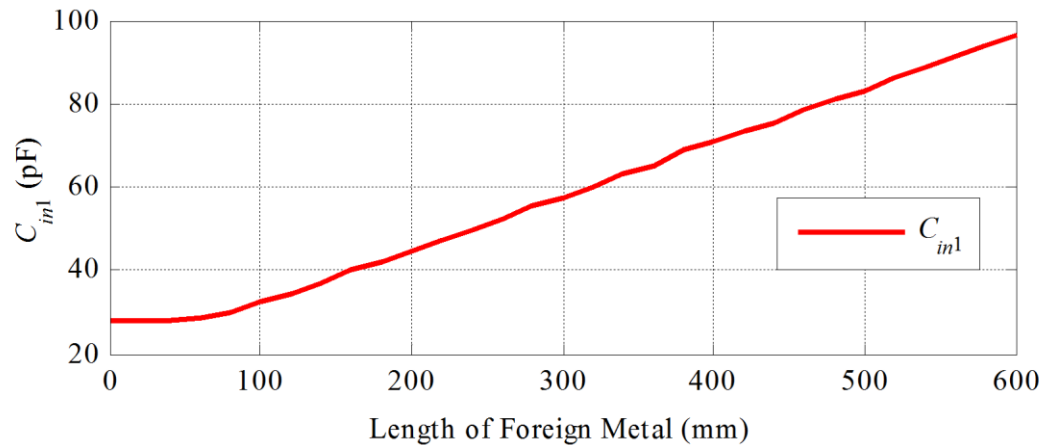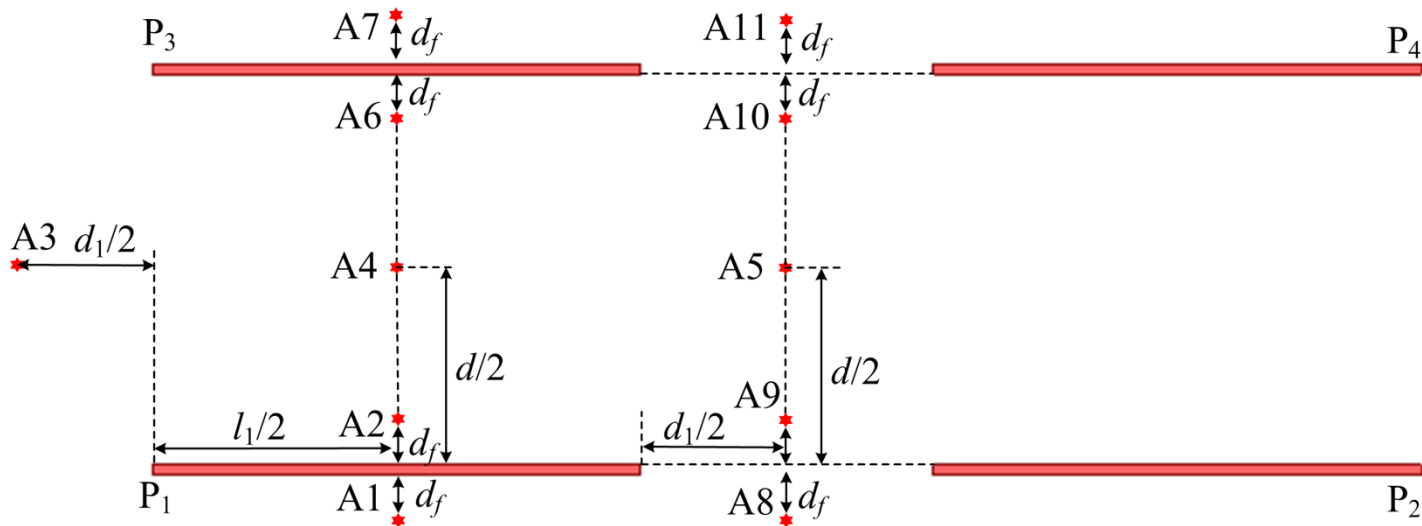

- Positions A5, A8, A9, A10, and A11 are sensitive positions
- The influence becomes significant with increasing metal size

# Circuit Model of Human Touch

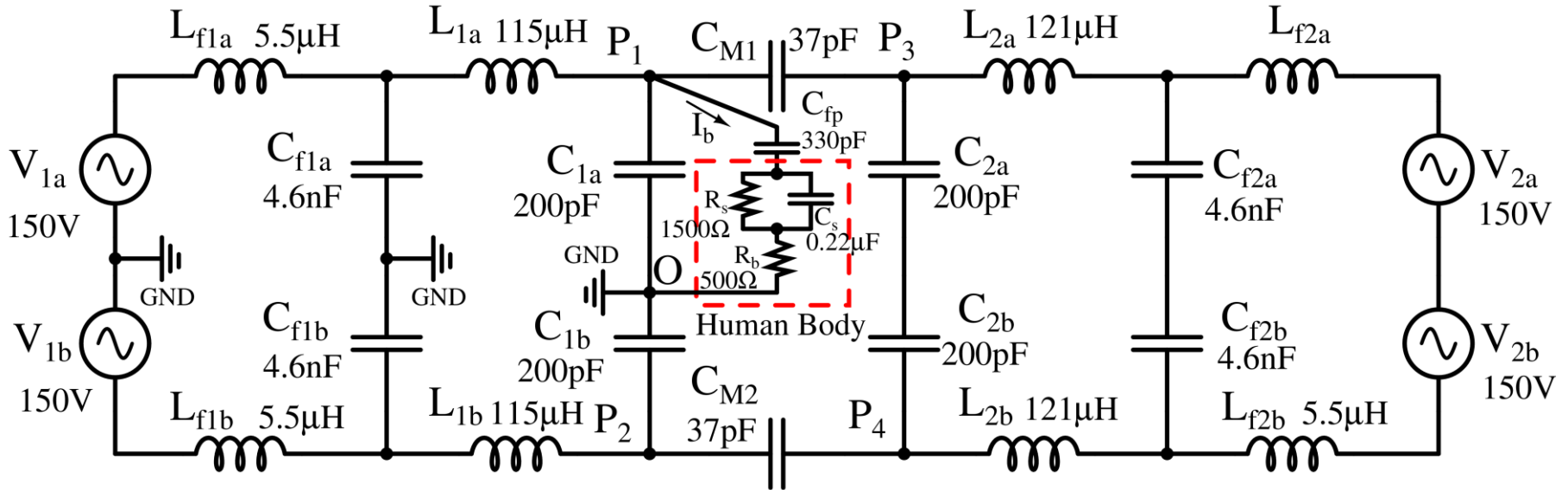

- At high frequency, human model is approximated to be 500Ω resistor (IEC)
- High-frequency (above 100 kHz) current has no neurological and cardiac problem (IEEE 95.1)
- Circuit simulation shows  $I_b=2.2$  A, which may cause heating problem
- IEEE C95.1 requires average energy density lower than 144J/kg in 6 minutes
- Safe with 100 ms protection mechanism






$$D = \frac{I_b^2 \times R_b \times t}{m} = \frac{2.2^2 \times 500 \times 0.1}{60} = 4.03 \text{ J/kg} < 144 \text{ J/kg}$$



# Final Comparison of CPT and IPT

	IPT	CPT
Switching frequency	85kHz	1MHz
Coupling field	Magnetic	Electric
Foreign objects (metal)	Will generate heat	Will not generate heat
Material	Litz wires, ferrites	Copper/Aluminum plates
Cost	High	Low
Safety	Good	Excellent
Size	Small	Large
Misalignment	Poor	Good
Efficiency	Excellent	Excellent
Voltage stress	Medium	High
Power level	High	Medium
Stationary or dynamic	Better for stationary	Both
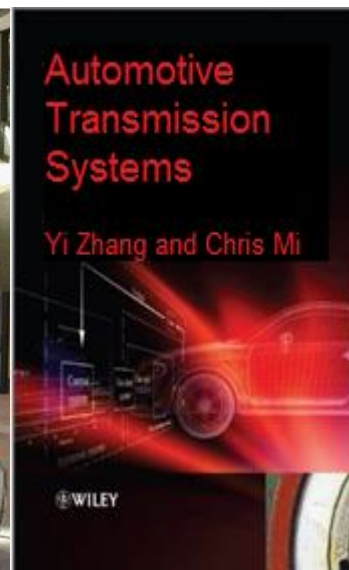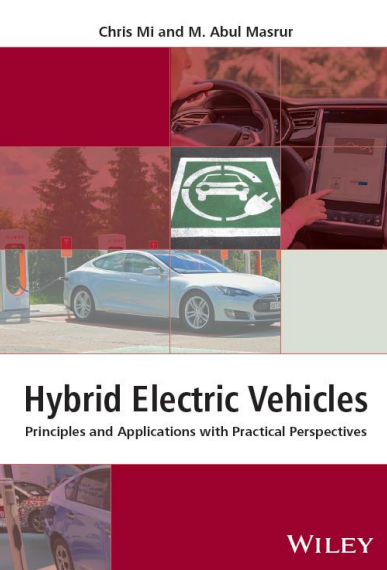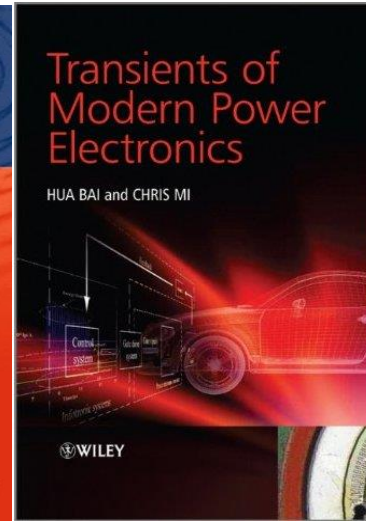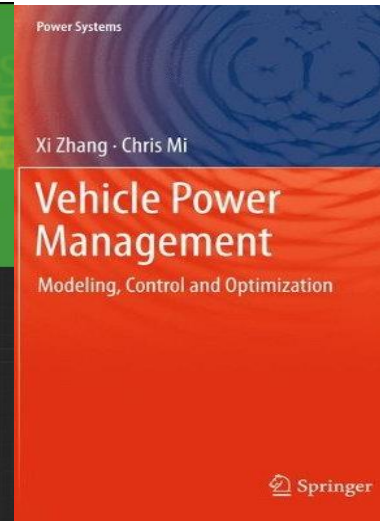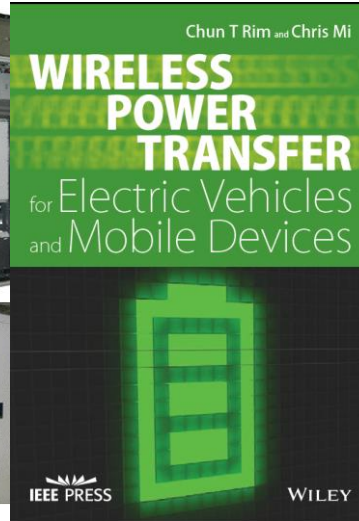
# We are committed to conduct research to improve performance, efficiency and safety




# Proud Sponsors





# Hardworking Students!

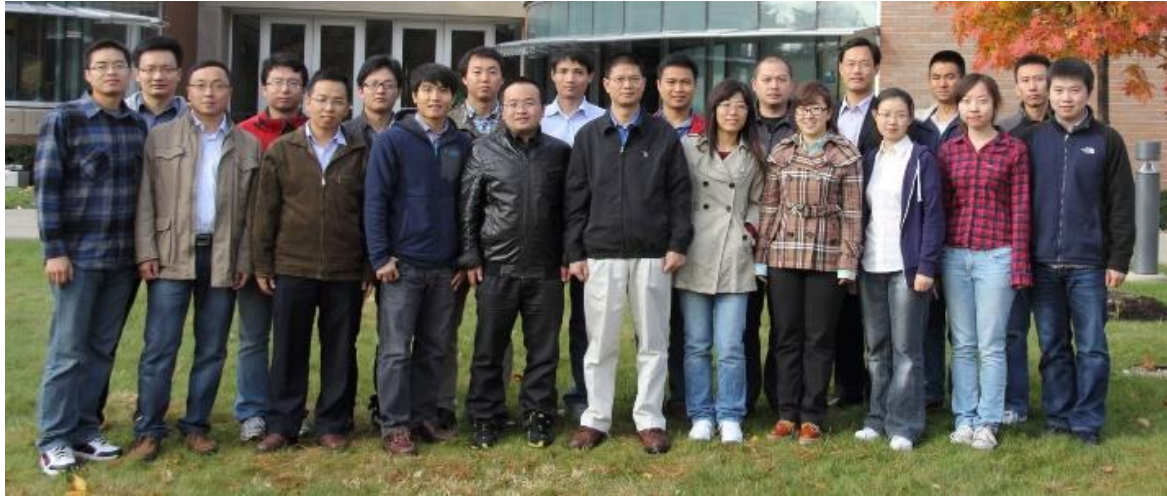

**Q&A**

**Thanks!**